

Simulating the ZetaSDR radio

Jason Leake

April 2019

1 Introduction

The ZetaSDR radio (LY1GP, 2007), designed by a Lithuanian radio amateur, call sign LY1GP, is a simple direct conversion radio receiver with a very small part count and forms the front end for a software defined radio. The output from it is an analogue inphase and quadrature signal, that allows the baseband to be extracted from several different forms of modulation, for example frequency modulation and quadrature amplitude modulation.

This program simulates the operation of the Tayloe mixer that forms the core of the ZetaSDR – the 74HC4052 (Motorola, 1996), and the Johnson counter that drives it, producing the response to a simulated amplitude modulated RF signal. I wrote the program to see what ideal time domain waveforms should look like on an oscilloscope as an informal aid to constructing and optimising the radio.

Whilst this document contains a back-of-an-envelope analysis of the operation of the mixer, the reader is referred to Soer (2007) for a far more thorough examination.

The source code for the simulation is `program.cpp`, and `plot.py` generates the plots from its CSV format output files. The program works on instantaneous samples of a simulated incoming signal using the transformations that key components apply to it, rather than employing a circuit solver.

The program was written for Ubuntu Linux is dependent upon several packages, which can be installed via:

```
sudo apt-get install make g++ librtfilter-dev python3 python3-matplotlib texlive-all
```

Generating this PDF document is achieved by:

```
make zetasdr.pdf
```

2 Operation of the ZetaSDR

The incoming RF electromagnetic signal induces a small electrical current in the antenna. The current passes across capacitor C6 (Figure 1) which acts as a high pass filter, blocking DC from passing from the receiver circuit to the antenna, which could otherwise cause problems with preamplifiers.

A 2.5 volt bias is applied to the RF signal by the voltage divider R1/R2 so that the signal oscillates around 2.5 volts instead of 0 volts. This means that the rest of the circuit is dealing with a signal

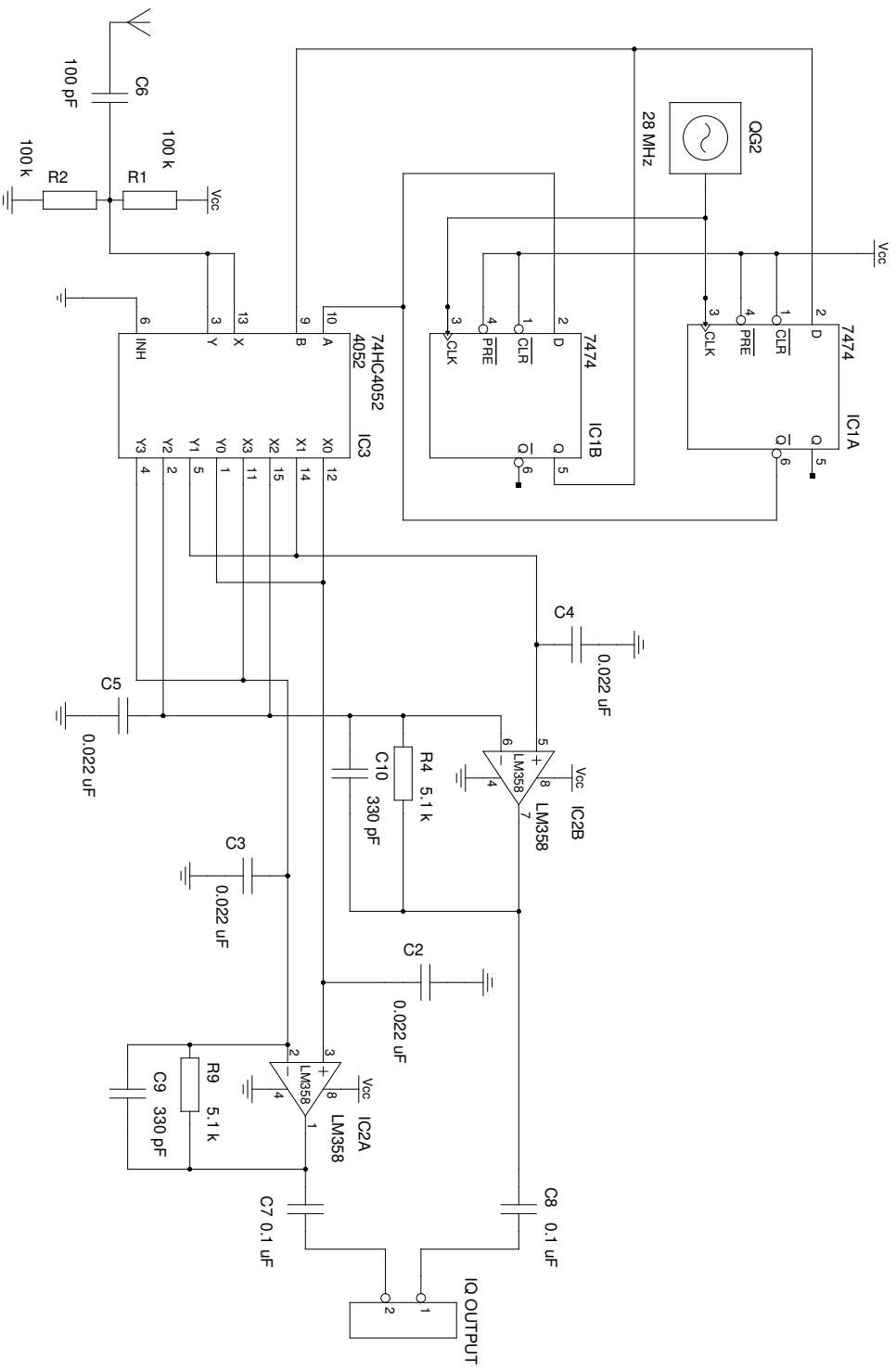


Figure 1: ZetaSDR schematic (after LY1GP (2007))

in the middle of its normal operating range instead of around 0 volts where non-linearity in the response will be great even if it can respond at all.

2.1 Tayloe quadrature product detector

The ZetaSDR uses a Tayloe quadrature product detector (Tayloe, 2013, 2001), often informally called a Tayloe mixer, to demodulate the signal. This is a type of quadrature sampling detector, a switching mixer that produces quadrature (IQ) signals. The ZetaSDR implementation uses a 74HC4052 analogue multiplexer/demultiplexer and capacitors to implement an integrator. It samples, averages and holds the RF signal on each quarter cycle, sending the first and third quarter samples to the I output, and the second and fourth quarter samples to the Q output.

The 74HC4052 is a twin channel analogue multiplexer/demultiplexer. One channel has an input, X, and switches it to one of four outputs, X0 \rightarrow X3 depending on the state of the digital inputs A and B (as shown in Table 1). If output Xn is enabled then the impedance between it and X is around 70 Ω (depending on supply voltage), and if not enabled then the path is open circuit. The device is bidirectional, but this is not relevant here, for the purposes of the ZetaSDR it is enough that the input from the antenna (X) is switched to one of the four outputs X1 \rightarrow X4. The other 74HC4052 channel has an input called Y, switching to Y1 \rightarrow Y4. The circuit uses both channels in parallel to halve the impedance seen across the device from about 70 Ω to 35 Ω .

A	B	X	Y
0	0	X0	Y0
0	1	X1	Y1
1	0	X2	Y2
1	1	X3	Y3

Table 1: Operation of 74HC4052

The inputs A and B are driven by a Johnson counter (also called a twisted ring counter) made from two D-type flip flops. This provides two binary signals, connected to A and B, that change on every clock cycle. The clock is supplied by the QG2 local oscillator. The counter operates as a 2 bit wide shift register, with the last bit value being inverted and fed into the first bit of the shift register on each clock cycle, so generating a repeating sequence 00, 01, 11, 10. The local oscillator runs at four times the frequency of the RF carrier, producing a new bit pattern in the Johnson counter, and thus switching the 74HC4052, on every quarter cycle of the RF carrier.

Hence, each of the four pairs of outputs X0/Y0, X1/Y1, X2/Y2 and X3/Y3 receive a quarter cycle of the RF signal. The outputs connect to the sampling capacitors that charge/discharge as the RF carrier signal is applied to them but hold their voltage when the corresponding 74HC4052 output is disabled and so in its high impedance state.

The amplitude of the RF carrier depends on the incoming signal strength and the quality of the antenna and preamplifier, so I picked an arbitrary value of 1 mV for the simulation program.

The waveform shapes produced by the simulation will be the same for smaller voltages, albeit with a smaller amplitude since the simulation does not model the noise in the system.

Since the local oscillator output is the Johnson counter clock, the flip flops making up the counter change when the local oscillator signal transitions from a voltage corresponding to logic 0 to logic 1. The simulation sets the logic 1 transition to a conventional 2.4 volts, and since the local oscillator has a swing of 5 volts, the clock occurs just below the midpoint on the local oscillator upswing.

Because the Johnson counter produces the sequence 00, 01, 11, 10, the first and third quarters of

 


Figure 2: Voltage on C2 and C3, ZetaSDR, when the local oscillator is in phase with the RF signal. The 74HC4052 switching leads the RF signal phase very slightly because its local oscillator derived clock changes logic state just below the midpoint on the local oscillator upswing.

the RF carrier cycle are selected using outputs X0 and X3 respectively, and the second and fourth using X1 and X2.

The voltage on the sampling capacitors C2 and C3 are shown in Figure 2. The local oscillator is set to have a range of 0–5 volts, and have its 0° point at the 0°, 90°, 180° and 270° positions of the RF carrier. In this idealised simulation the Johnson counter therefore changes state very slightly before this point, when the local oscillator voltage is rising through 2.4 volts.

In practice, it is unlikely that the local oscillator will be in phase with the RF carrier, and there will be small delays in the Johnson counter logic and the 74HC4052 operation.

The two sampling capacitors are also connected to the differential inputs of an active low pass filter that both amplifies and filters the difference between the two voltages. In the simulation, the low pass filters have an infinite input impedance. The final output voltage is shown on the lower plot in Figure 2 – the effect of taking the difference between the two signals, which will be normally be similar but of opposite polarity, is to produce a signal of double the size of each. The corresponding voltages on the other pair of capacitors, C4 and C5, are shown in Figure 3.

In the LY1GP (2007) schematic, a 28.322 MHz local oscillator is specified, but the simulation uses a 28 MHz oscillator and hence a 7 MHz radio signal.

The sharp transitions and the short-lived spikes will be attenuated by the active low pass filter stage. Hence, the demodulator is producing an output where the I signal is sampled at two points in the carrier cycle 180° apart, and the Q signal is the signal sampled 90° on from those points in much

 


Figure 3: Voltage on C4 and C5, ZetaSDR, when the local oscillator is in phase with the RF signal

the same way that the multiplication by the respective local oscillator does it in a conventional multiplying IQ mixer.

Hence, if the amplitude or phase of the signal does not change rapidly during the sampling and we ignore the quarter cycles where the voltage on the capacitors is changing, then for the I signal, the voltage at capacitor C2 in Figure 2 is

$$s_1 = A \cos(\theta) \sin(\omega_b t)$$

where:

ω_b is the baseband frequency in radians per second

θ is the phase difference between the carrier and the Johnson counter transitions (and hence the 74HC4052 switching)

The voltage across C3 is:

$$\begin{aligned} s_2 &= A \cos(\theta) \sin(\pi + \omega_b t) \\ &= -A \cos(\theta) \sin(\omega_b t) \end{aligned}$$

Because the active filter is the difference between the two voltages, the filter output is:

 


Figure 4: Voltage on C2 and C3 in the ZetaSDR, when the local oscillator is in phase with the RF carrier, and the 7 MHz carrier is amplitude modulated at 100 kHz

$$I = s_1 - s_2 = 2A\cos(\theta)\sin(\omega_b t) \quad (1)$$

Hence, the difference into the active low pass filter, ignoring the high frequency portion which results when one of the capacitors is tracking the output from the 74HC4052 rather than holding its voltage, is $2A\sin(\theta)\sin(\omega_b t)$.

By the same reasoning, the Q signal formed from the voltage difference between C4 and C5 is:

$$Q = 2A\sin(\theta)\sin(\omega_b t) \quad (2)$$

The corresponding plots for a modulated signal are shown in Figures 4 and 5. Many more RF cycles are shown in these plots, and the 7 MHz carrier is amplitude modulated at 100 kHz. Although this is above the audio range, it allows several AM cycles can be accommodated

In practice, the 74HC4052 switching will usually be more out of phase with the RF carrier signal, and so something such as Figure 6 (and Figure 7 for the other pair of capacitors) is more likely. The modulated versions of these plot, over a larger number of carrier cycles, are shown in Figures 8 and 9 are obtained.

Figure 10 shows the I and Q signals through a low pass filter and then combining them to extract the baseband. Because of the unusually high modulation frequency and signal strength used in the simulation, a 500 kHz 2nd order zero gain low pass Butterworth filter is used instead of the higher gain and lower frequency cutoff active low pass filters in the ZetaSDR radio.

 


Figure 5: Voltage on C4 and C5, when the local oscillator is in phase with the RF carrier, and the 7 MHz carrier is amplitude modulated at 100 kHz

 


Figure 6: Voltage on C2 and C3 in the ZetaSDR, when the local oscillator leads the RF carrier by 35°

 


Figure 7: Voltage on C4 and C5 in the ZetaSDR, when the local oscillator leads the RF carrier by 35°

 


Figure 8: Voltage on C2 and C3 in the ZetaSDR, when the local oscillator leads the carrier by 35° , and the 7 MHz carrier is amplitude modulated at 100 kHz

 


Figure 9: Voltage on C4 and C5 in the ZetaSDR, when the local oscillator leads the carrier by 35° , and the 7 MHz carrier is amplitude modulated at 100 kHz

3 Comparison with an ideal multiplying IQ mixer

A sinusoidally amplitude modulated RF signal, with a 100% modulation depth, double-sideband and full-carrier, is described by:

$$S = A \sin(\omega_b t) \sin(\omega_c t) \quad (3)$$

where:

A is the signal amplitude
 ω_b is the baseband frequency
 ω_c is the carrier frequency
 t is time

In a conventional multiplying IQ mixer, the I signal is produced by mixing with a local oscillator with a phase difference θ :

 


Figure 10: ZetaSDR response to a 100 kHz amplitude modulated signal, when the local oscillator is 35° ahead of the RF carrier. Because of the high input signal amplitude and the high modulation frequency, the active low pass filters have been replaced with a 2^{nd} order low pass filter, but with unity gain and a cutoff frequency of 500 kHz.

$$\begin{aligned}
I &= A \sin(\omega_b t) \sin(\omega_c t) \sin(\omega_c t + \theta) \\
&= A \sin(\omega_b t) \frac{\cos(\theta) - \cos(2\omega_c t - \theta)}{2} \\
&= \frac{A \sin(\omega_b t) \cos(\theta)}{2} - \frac{\cos(2\omega_c t - \theta)}{2}
\end{aligned}$$

Because

$$\sin(\alpha) \sin(\beta) = \frac{\sin(\alpha + \beta) - \sin(\alpha - \beta)}{2}$$

The Q signal is produced by mixing the incoming RF signal with a similar local oscillator signal that is 90° out of phase with the I local oscillator:

$$\begin{aligned}
Q &= A \sin(\omega_b t) \cos(\omega_c t) \sin(\omega_c t + \theta) \\
&= A \sin(\omega_b t) \frac{\sin(2\omega_c t + \theta) + \sin(\theta)}{2} \\
&= \frac{A \sin(\omega_b t) \sin(2\omega_c t + \theta)}{2} + \frac{A \sin(\omega_b t) \sin(\theta)}{2}
\end{aligned}$$

Because

$$\cos(\alpha) \sin(\beta) = \frac{(\sin(\alpha + \beta) - \sin(\alpha - \beta))}{2}$$

In both cases, a low pass filter will remove the sum portion of the signal at frequency $2\omega_c$ leaving only the difference frequency:

$$\begin{aligned}
I &= \frac{A \sin(\omega_b t) \cos(\theta)}{2} \\
Q &= \frac{A \sin(\omega_b t) \sin(\theta)}{2}
\end{aligned}$$

These two equations are of the same form as Equations 1 and 2, the ones for the Tayloe quadrature product detector, demonstrating that it operates as an IQ mixer.

The results of the simulation of an ideal multiplying IQ mixer are shown in Figures 11–13 for comparison with the Tayloe detector simulation plots above.

Like the IQ mixer output, the Tayloe detector in the ZetaSDR produces sum and difference frequencies. The high frequency portion of detector output signal is at $2\omega_c$, since the rapidly varying portion gets through two cycles for each cycle of the RF carrier, although in this case there are

additional harmonics. The detector capacitors are intended to form an RC low pass filter with the resistance through the 74HC4052 to remove the sum frequency component (the Tayloe mixer minimises the use of resistors to reduce noise). However, the ZetaSDR has an additional active low pass filter, so this filter is redundant, and for this reason the detector capacitors can be deleted.

The cutoff frequency of the RC circuit is about 85 kHz if the aggregate resistance through the pair of 74HC4052 channels in parallel is 35 Ω and the impedance of the antenna is 50 Ω . Tayloe (2013) says that effective resistance for filter calculations is quadrupled if the signal is only connected for a quarter of the time, but my simulation works at a small time step level, so still sees the “instantaneous” cutoff at 85 kHz when the capacitor is connected to the signal, and the capacitor voltage frozen when it is disconnected.

The modulation frequencies used by the simulation are 83 kHz and 100 kHz, as a not entirely ideal compromise between being strongly affected by this RC filter and being a sufficiently high frequency to allow the plots to show at least one modulation cycle.

Perhaps the greatest weakness of the design is that it relies upon the mixer to emphasise the tuned frequency over adjacent ones. Perhaps this is not such a problem in practice if the antenna can be tuned.

But to investigate this further, Figures 14 and 15 show simulations for a pair of signals close to each other and the ZetaSDR radio tuned to one or other signals. The signal parameters are shown in Table 2. The conclusion from these simulations is that the adjacent signal introduces very considerable distortion on the demodulated signal that the radio is tuned to, although Figures 16 and 17 show that an ideal IQ mixer without any additional tuning capability also produces similarly distorted results.

Signal	Carrier frequency	Amplitude modulation frequency
Signal 1	7 MHz	100 kHz
Signal 2	7.5 MHz	83 kHz

Table 2: Signals used in examining adjacent signal response

References

- LY1GP (2007), *ZetaSDR for 40m band*
<http://www.qrz.lt/ly1gp/SDR/>
- Motorola (1996), *Analog Multiplexers/Demultiplexers High-Performance Silicon-Gate CMOS*,
<http://www.om3bc.com/datasheets/74HC4051.PDF>
- Soer M (2007), *Analysis and comparison of switch-based frequency converters*, MSc. thesis, University of Twente, https://essay.utwente.nl/58276/1/scriptie_Soer.pdf
- Tayloe, D (2001), *Product detector and method therefor* – *United States Patent No 6230000*, United States Patent and Trademark Office,
<https://patentimages.storage.googleapis.com/ec/5f/c214501bb441f1/US6230000.pdf>
- Tayloe, D (2013), *Ultra Low Noise, High Performance, Zero IF Quadrature Product Detector and Preamplifier*,
https://wparc.us/presentations/SDR-2-19-2013/Tayloe_mixer_x3a.pdf

 


Figure 11: I/Q outputs using an ideal multiplying IQ mixer, when the local oscillator is in phase with the RF carrier, and the 7 MHz carrier is amplitude modulated at 100 kHz

 


Figure 12: I/Q outputs using an ideal multiplying IQ mixer when the local oscillator leads the carrier by 35° , and the 7 MHz carrier is amplitude modulated at 100 kHz

 


Figure 13: I/Q outputs using an ideal multiplying IQ mixer, when the local oscillator is 35° ahead of the RF carrier, and with the I/Q signals passed through a 2^{nd} order low pass filter with a cutoff of 400 kHz to remove the $2\omega_c$ signal. Compare this ideal case with Figure 10.

 


Figure 14: I and Q outputs from the ZetaSDR with the local oscillator starting 35° ahead of the carrier. The second order low pass filter has a cutoff of 400 kHz. The signals present described in Table 2, with the local oscillator tuned to Signal 1.

 


Figure 15: I and Q outputs from the ZetaSDR tuned to Signal 2 in Table 2, and starting starting 35° ahead of the carrier.

 


Figure 16: I and Q outputs from an ideal multiplying IQ mixer with the local oscillator tuned to Signal 1 in Table 2, and starting starting 35° ahead of the carrier.

 


Figure 17: I and Q outputs from an ideal multiplying IQ mixer. local oscillator is tuned to Signal 2 in Table 2, and starting starting 35° ahead of the carrier.